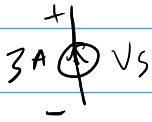


Chapter 8



Current Source




Supply a fixed current, but the voltage across it can change

Ideally, a current source internal resistance is very large, therefore, the internal resistance of a current source is infinite.

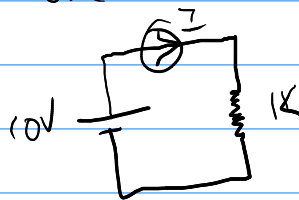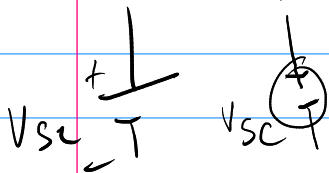
Voltage source can supply a fixed voltage however the current will be variable or depends on the load



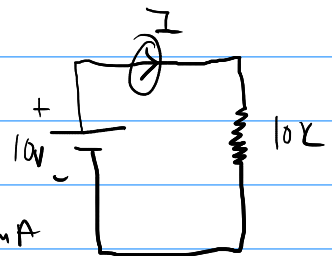
$$I = \frac{V}{R} = \frac{10V}{1k} = 10mA$$



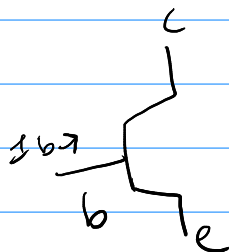The internal individual resistance of a voltage source is very small, so ideally it is zero, short




Transistor

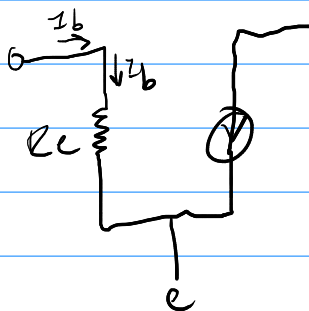

model


$$h_{ge} = 20^6$$

Source Transformation

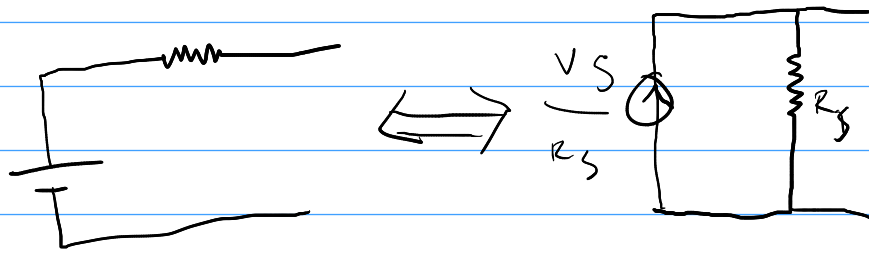

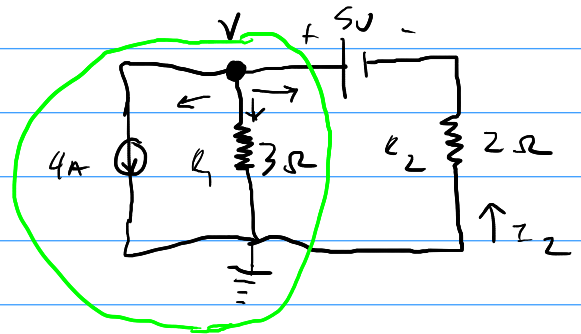Example: Determine the current I_2 in the circuit below

$$6 \left(\frac{V-0}{3} + \frac{V-5}{2} + 4 \right) = 0$$



$$2V + 3(V-5) + 24 = 0$$


$$5V - 15 + 24 = 0$$

$$5V = -24 + 15 = -9$$

$$V = \frac{-9}{5} = -1.8V$$

$$I_1 = \frac{V-5}{2} = \frac{-1.8-5}{2} = -3.4A$$

$$I_2 = +3.4A$$

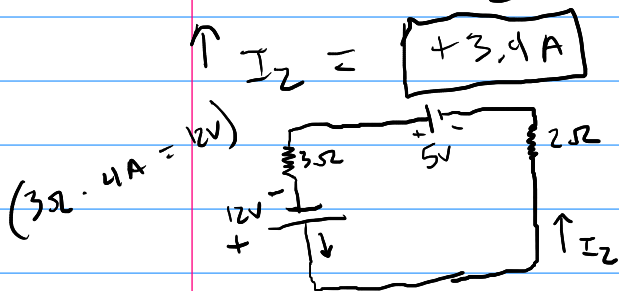

$$-12 + 2I_2 - 5 + 3I_2 = 0$$

$$5I_2 = 17$$

$$I_2 = \frac{17}{5} = 3.4A$$

Example: find I_L

$$\frac{V-32}{8} - 6 + \frac{V}{24} + \frac{V}{14} = 0$$

$\frac{3 \times 8}{4 \times 2}$ $\frac{7 \times 7}{7 \times 7}$


$3 \times 8 \times 7$

$$V \left(\frac{1}{8} + \frac{1}{24} + \frac{1}{14} \right) = 10$$

$$\frac{V}{8} - \frac{32}{8} - 6 + \frac{V}{24} + \frac{V}{14} = 0$$

$$V \left(\frac{1}{8} + \frac{1}{24} + \frac{1}{14} \right) = 10$$

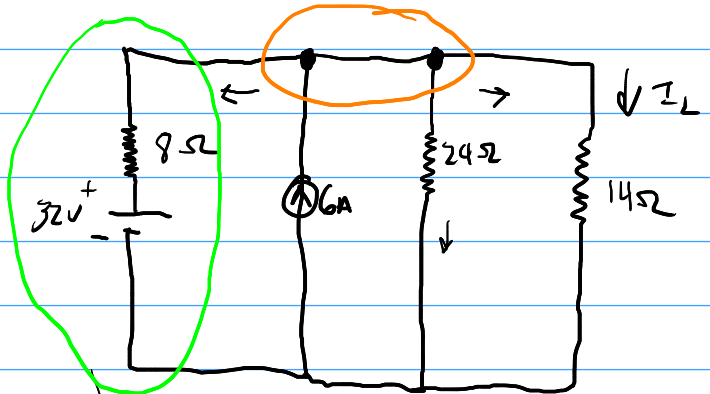
$$V = \frac{10}{\frac{1}{8} + \frac{1}{24} + \frac{1}{14}} = 42V$$




$$21(V-32) - 6 \times 7 \times 8 \times 3$$

$$+7V + 12V = 0$$

$$I_L = \frac{42V}{14} = 3A$$

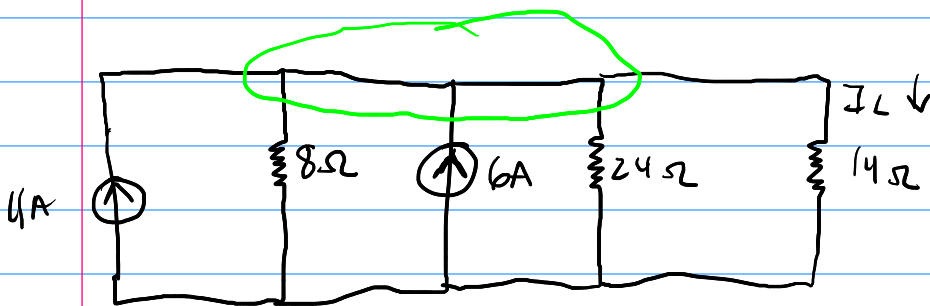

$$\frac{8 \times 24}{8 + 24} = 6\Omega$$

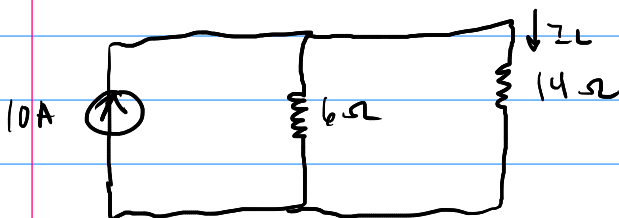

$$I_L = \frac{6}{6 + 14} (10A) = 3A$$

Network Theorem

1- Super position

The current through, or voltage across an element in linear Network equal to the algebraic sum of the currents or voltages produced independently by each source

Example:


$$\frac{V-30}{4} - 4 + \frac{V}{6} = 0$$

$$3(V-30) - 48 + 2V = 0$$

$$3V - 90 - 48 + 2V = 0$$


$$5V = 90 + 48 \quad V = \frac{138}{5} = 27.6V$$

$$I_1 = \frac{27.6V}{6\Omega} = 4.6A$$

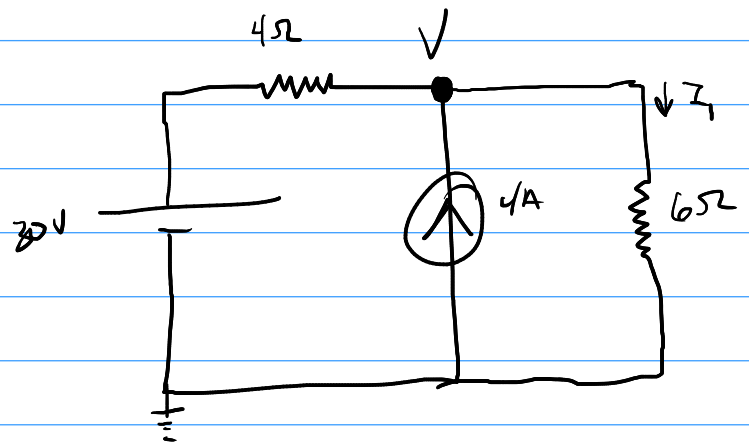


Super Point

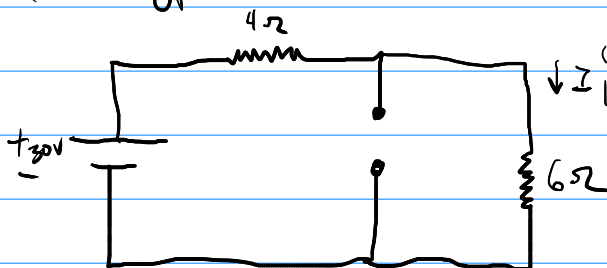1. Turn off the current source, replace it by an open



$$I_1' = \frac{30}{4+6} = 3A$$

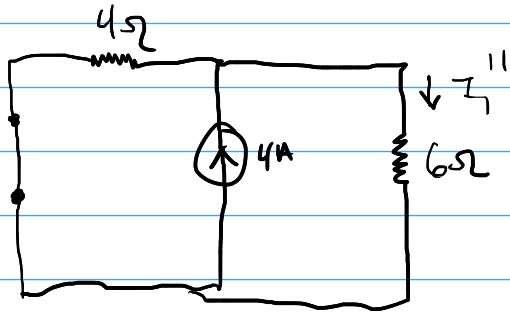2. Turn off 30V voltage source, replace it by a short



$$I_1' = \frac{4}{4+6} (4A) = 1.6A$$

$$I_{1T} = \overset{\downarrow I}{I_1} + \overset{\downarrow I'}{I_1'} = 3A + 1.6A = 4.6A$$