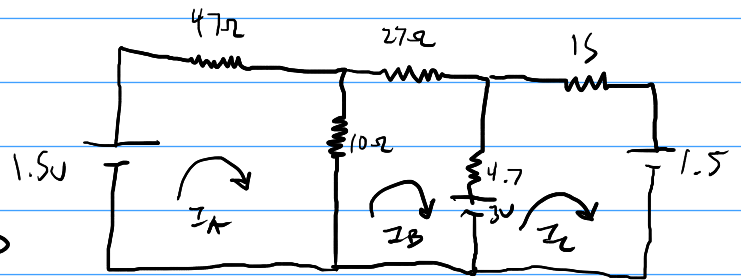


$$-1.5 + 4.7 + 10(I_A - I_B) = 0$$

$$27I_B + 4.7(I_B - I_C) + 3 + 10 = 0$$

$$15I_C + 1.5 - 3 + 4.7(I_C - I_B) = 0$$



$$57I_A - 10I_B + 0I_C = 1.5$$

$$-10I_A + 41.7I_B - 4.7I_C = -3$$

$$0I_A - 4.7I_B + 19.7I_C = 1.5$$

$$\begin{bmatrix} 57 & -10 & 0 \\ -10 & 41.7 & -4.7 \\ 0 & -4.7 & 19.7 \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 1.5 \\ -3 \\ 1.5 \end{bmatrix}$$

$$a = \begin{bmatrix} 57 & -10 & 0 \\ -10 & 41.7 & -4.7 \\ 0 & -4.7 & 19.7 \end{bmatrix}$$

$$b = \begin{bmatrix} 1.5 \\ -3 \\ 1.5 \end{bmatrix}$$

$$a/b$$

$$I_A = 30.5 \text{ mA}$$

$$I_B = 23.7 \text{ mA}$$


$$I_C = 3.18 \text{ mA}$$

228 chapter 9

$$\frac{V_A - 30}{82} + \frac{V_A - 40}{68} + \frac{V_A}{47 + 100} = 0$$


$$\frac{V_A}{82} - \frac{30}{82} + \frac{V_A}{68} - \frac{40}{68} + \frac{V_A}{147} = 0$$
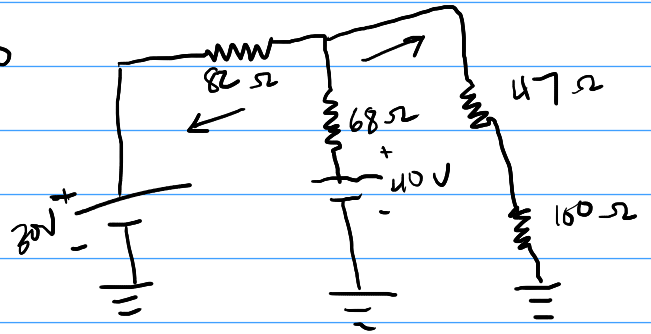
$$V_A \left\{ \frac{1}{82} + \frac{1}{68} + \frac{1}{147} \right\} = \frac{30}{82} + \frac{40}{68}$$



Maximum Power transfer

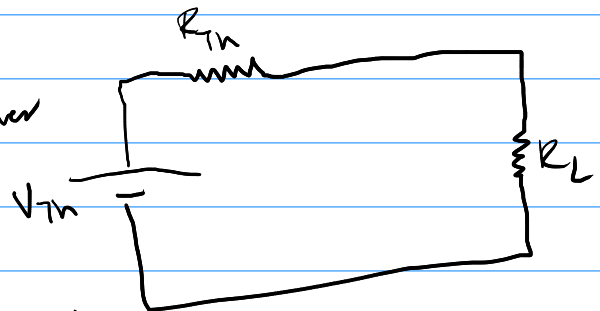A load will receive maximum power from a linear network when its total resistance value is exactly equal to the Thevenine resistance of the network



$$R_L = R_{Th}$$

$$Power = \frac{V_{RL}^2}{R_L}$$

$$V_{RL} = \frac{R_L}{R_L + R_{Th}} V_{Th}$$



$$P_{RL} = \frac{V_{RL}^2}{R_L} = \frac{\left(\frac{R_L}{R_L + R_{Th}} V_{Th} \right)^2}{(R_L + R_{Th})^2 R_L}$$

$$\frac{dP_L}{dL} = 0$$

$$P_x = \frac{x^2 V_{Th}^2}{(x + R_{Th})^2 x}$$

$$\frac{d}{dx} \left[\frac{f(x)}{g(x)} \right] = \frac{f'g - g'f}{g^2} \quad \frac{dP_x}{dx} =$$

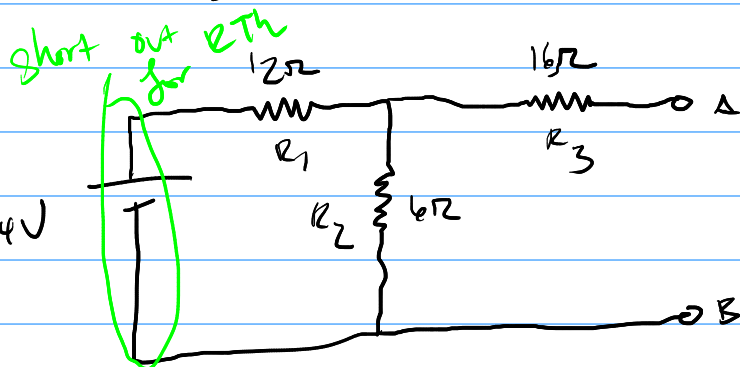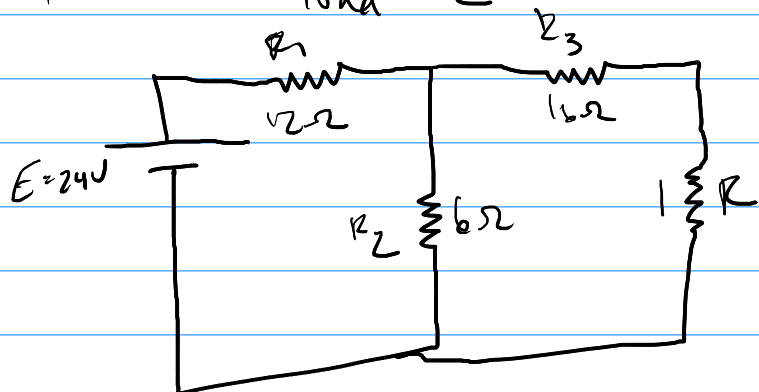Example: Determine R for maximum Power transfer to the load R



No current to R_3

$$V_{R_3} = I \cdot R_3 = 0$$

$$V_{AB} = V_{R_2}$$


$$V_{AB} = V_{R_2} = \frac{6}{6+12} (24) = 8V$$

$$V_{Th} = 8V$$

$$R_{Th} = R_{AB} = R_1 \parallel R_2 + R_3$$

$$= 12\Omega \parallel 6\Omega + 16\Omega =$$

$$\frac{(12)(6)}{12+6} + 16 = 20\Omega$$

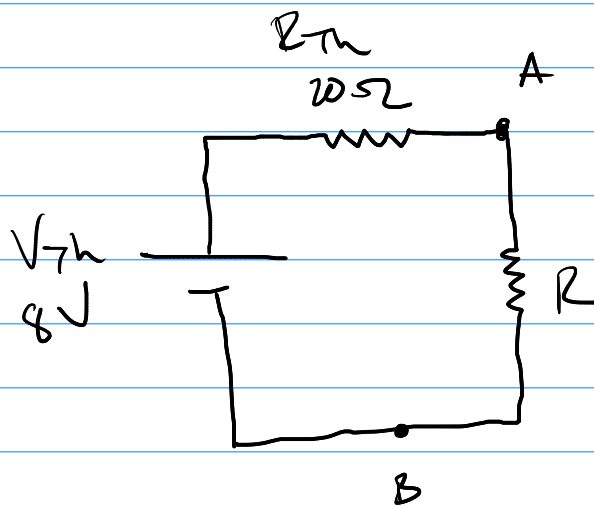

$$R = R_{Th} = 20\Omega$$

$$V_R = \frac{V_{Th}}{2}$$

$$I_R = \frac{V_{Th}}{R_{Th} + R} = \frac{V_{Th}}{2R}$$

$$P_R = \frac{V_{Th}^2}{4R}$$

$$P_R = I_R^2 R$$

$$= \left(\frac{V_{Th}}{2R} \right)^2 R = \frac{V_{Th}^2}{4R}$$