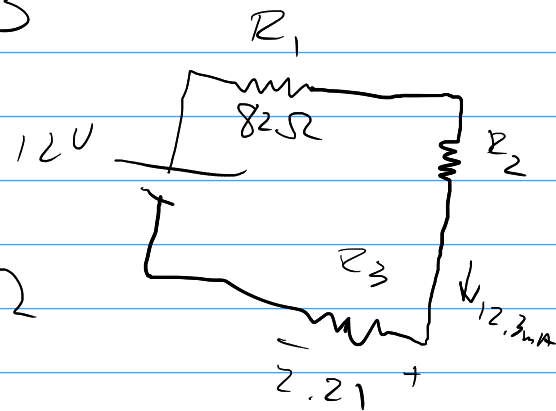


Chapter 5

Determine V_{R1} , R_2 , & R_3


$$V = I \cdot R$$

$$R_3 = \frac{V_{R3}}{I} = \frac{2.21}{12.3 \text{ mA}} = 180 \Omega$$



$$R_T = \frac{12}{12.3 \text{ mA}}$$
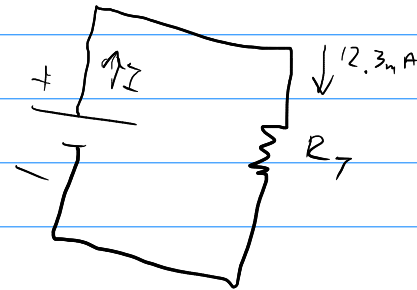
$$V_{R1} = I \cdot R_1 = (12.3 \text{ mA})(82)$$



$$-12 + V_{R1} + V_{R2} + V_{R3} = 0$$

$$V_{R2} = 12 - (82)(12.3 \text{ mA}) - 2.21$$

$$R_2 = \frac{0}{12.3 \text{ mA}} = 714 \Omega$$


find R_1, R_2, R_3

R_2

$$P_2 = I^2 R_2 = \frac{V_{R_2}}{R_2} = I \cdot V_{R_2}$$

$$R_2 = \frac{P_2}{I^2} = \frac{22 \text{ mW}}{(10 \text{ mA})^2} = \frac{22 \cdot 10^{-3}}{10 \cdot 10^{-3}}$$
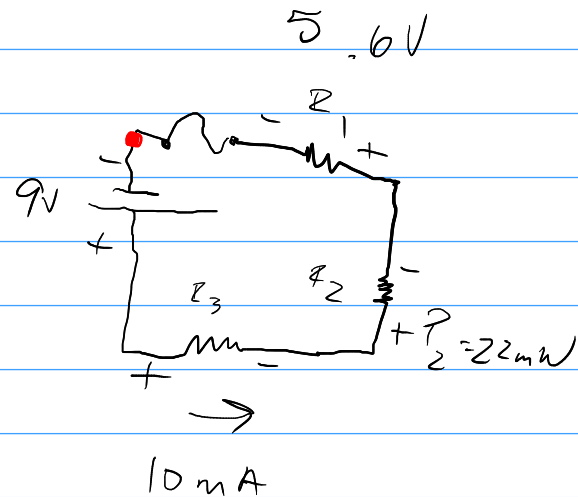
$$= \frac{22 \cdot 10^{-3}}{(0.01)^2} = \frac{22 \cdot 10^{-3}}{10^{-4}} = 22 \cdot 10^1 = 220 \Omega$$



$$R_1 = \frac{V_{R_1}}{I} = \frac{5.6}{10 \text{ mA}} = 560 \Omega$$

$$R_3 \quad -9 + V_{R_3} + V_{R_2} + V_{R_1} = 0$$

$$V_{R_3} = 9 - V_{R_2} - V_{R_1} = 9 - I R_2 - 5.6$$




$$= 9 - (10 \text{ mA})(220 \Omega) - 5.6$$

$$= 9 - 2.2 - 5.6$$


Chapter 6

Parallel circuits

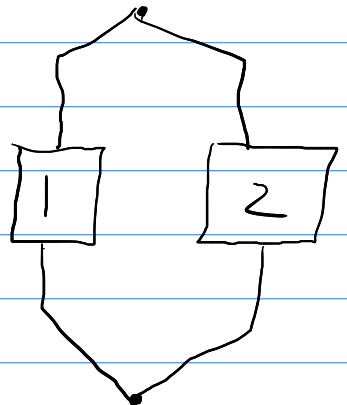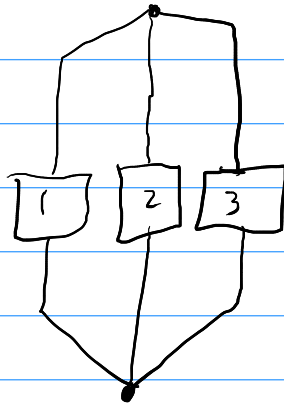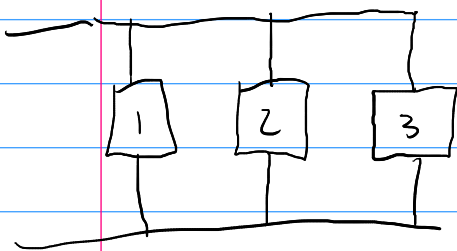Two elements, branches, or network are in parallel if they have two points in common.



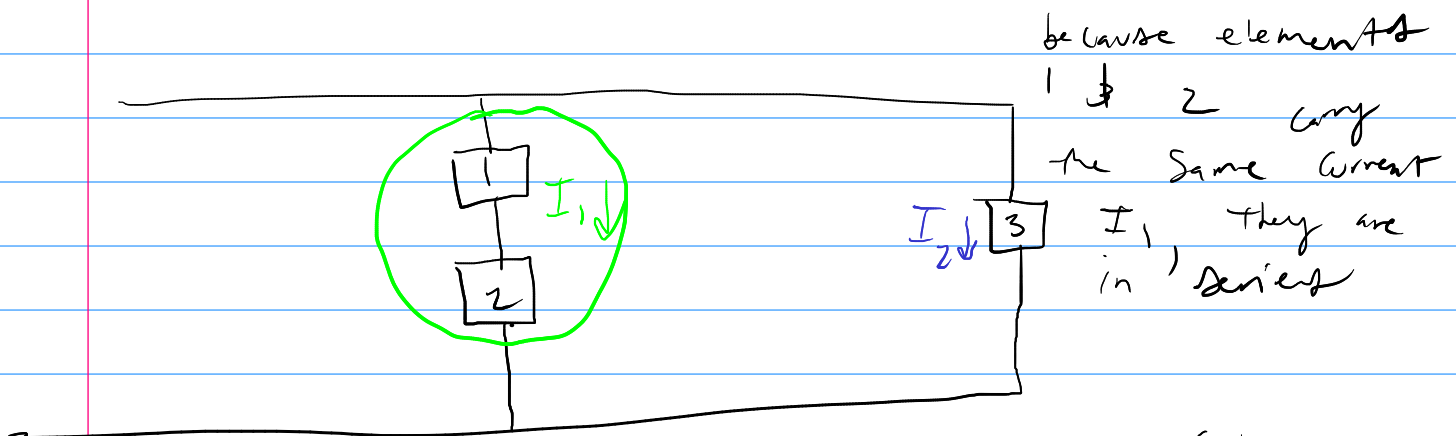two elements in parallel have the same voltage




because elements 1 & 2 carry the same current I_1 , they are in series

$$V_{R_3} = 12V$$

$$R_3 = 3k$$
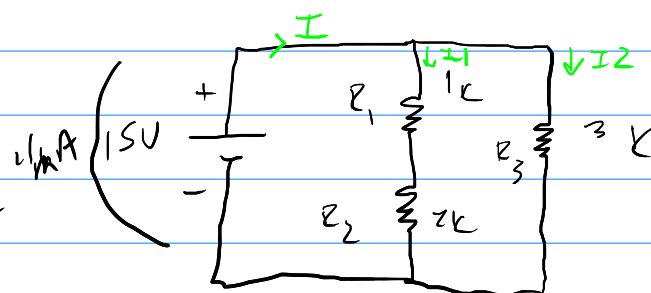
$$I_2 = \frac{V_{R_3}}{R_3} = \frac{12V}{3k} = 4mA$$



$$I_1 = \frac{15V}{3k} = 5mA$$

$$V_{R_1} = I_1 R_1 = (5 \text{ mA}) (1 \text{ k}) = 5 \text{ V}$$

Kirchoff's Current Law (KCL)

The algebraic sum of all currents entering or leaving a junction is zero.

The sum of currents entering a junction must be equal to the sum of currents leaving the junction


$$\text{Entering} = 2\text{A} + 1\text{A} + 4\text{A} = 7\text{A}$$

Entering a node = -

Leaving a node = +

$$-2 - 1 - 4 + I = 0$$

$$I = 2 + 1 + 4 = 7\text{A}$$

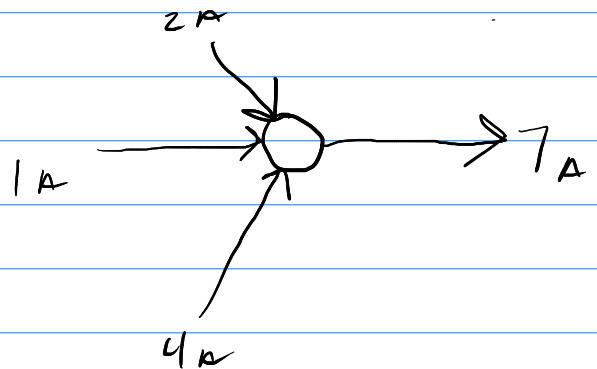

$$I_3 = I_1 + I_2 = 3\text{A} + 2\text{A} = 5\text{A}$$

$$I_3 + I_5 = I_4$$

$$5\text{A} + 1\text{A} = I_4 = 6\text{A}$$

