

**Lab 3**  
**Logic Circuits (EET 241)**  
**Total Points: 100**

**Objective:** Software simulation of binary addition, binary subtraction, even parity and odd parity.

**Materials Needed:** Logisim (you only need to do software simulation for this lab)

**Theory:** Binary arithmetic is essential in all digital computers and in many other types of digital systems. To understand digital systems, you must know the basics of binary addition and subtraction.

**Binary Addition:**




Four Basic Rules of Binary Addition:


$$\begin{array}{ll} 0 + 0 = 0 & \text{sum} = 0, \text{carry} = 0 \\ 0 + 1 = 1 & \text{sum} = 1, \text{carry} = 0 \\ 1 + 0 = 1 & \text{sum} = 1, \text{carry} = 0 \\ 1 + 1 = 10 & \text{sum} = 0, \text{carry} = 1 \end{array}$$

Notice that  $1 + 1 = 10$ , when binary numbers are added, it creates a sum of 0 in a given column and a carry of 1 over to the next column to the left.

$$011 + 001 = ?$$

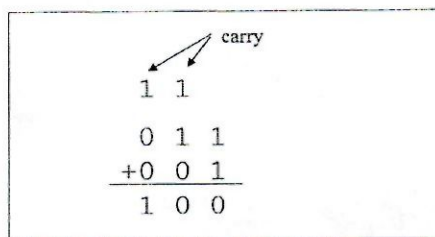

**Binary Subtraction**

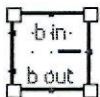

Four Basic Rules of Binary Subtraction:

$$\begin{array}{l} 0 - 0 = 0 \\ 1 - 1 = 0 \end{array}$$

$$1 - 0 = 1$$

$$0 - 1 = 1 \text{ with a borrow of 1; } 10 - 1 = 1$$

Notice that, a borrow is required in binary only when you try to subtract a 1 from a 0. In this case, when a 1 is borrowed from the next column to the left, a 10 is created in the column being subtracted.

$$11 - 01 = ?$$


	1	1
-	0	1
<hr/>		
	1	0

No borrow is required

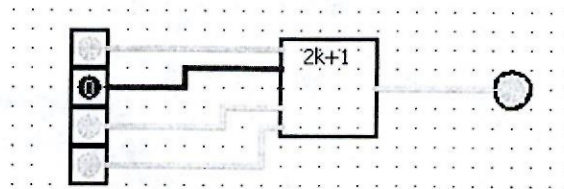
**Odd parity Gate:**




Odd Parity gate will emit 1 if there are an odd number of 1 input.



**Even parity gate:**

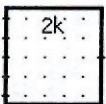

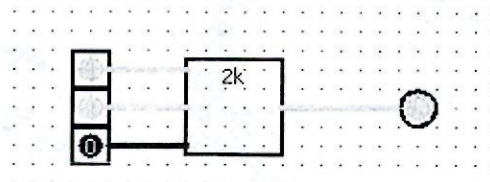Even Parity gate will emit 1 if there are an even number of 1 input.



Procedure:

1. You should watch the lectures posted on the mediasite where I discussed lab 3 in detail.
2. Connect **Adder** with input and output. Test the output for different combination of inputs. Tabulate the results on 1-1 (for the given input).
3. Connect **Subtractor** with input and output. Test the output for different combination of inputs. Tabulate the results on 1-2 (for the given input).
4. Connect **odd parity gate** with input and output. Test the output for different combination of inputs. Tabulate the results on 1-3 (for the given input).
5. Connect **even parity gate** with input and output. Test the output for different combination of inputs. Tabulate the results on 1-4 (for the given input).

## Lab 3 report

Name: *Derek White*

Data and Observations:



Table 1-1 Binary Addition

1000 + 1111	1011
1001 + 1111	11000

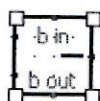


Table 1-2 Binary Subtraction

1111 - 1000	0111
1000 - 0100	0100



Table 1-3 Odd parity Gate

110101	0
100001	0

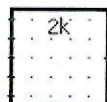


Table 1-4 Even parity Gate

110101	1
100001	1

### Submission Process

You should name Logisim file as lab3.circ. You just need to submit lab report and Logisim file (lab3.circ). You do not need to submit tutorial or procedure. I would suggest you create a folder and name it as Lab3 and copy your lab3 report and lab3.circ. Then you will zip the Lab3 folder. Finally, upload the zipped Lab3 file on the Canvas.