

Report for Experiment 5

Name _____
Date _____
Class _____

ABSTRACT:

DATA:

Table 5-1


Component	Listed Value	Measured Value
R_1	2.7 k Ω	

Table 5-2

Measured value of		
Resistance	Voltage	Current
k Ω	V	mA
Computed Power		
$P = IV$	$P = I^2 R$	$P = \frac{V^2}{R}$
mW	mW	mW

Table 5-3

Variable Resistance Setting (R_2)	V_1 (measured)	V_2 (measured)	Power in R_2 $P_2 = \frac{V_2^2}{R_2}$
0.5 k Ω			
1.0 k Ω			
2.0 k Ω			
3.0 k Ω			
4.0 k Ω			
5.0 k Ω			
7.5 k Ω			
10.0 k Ω			

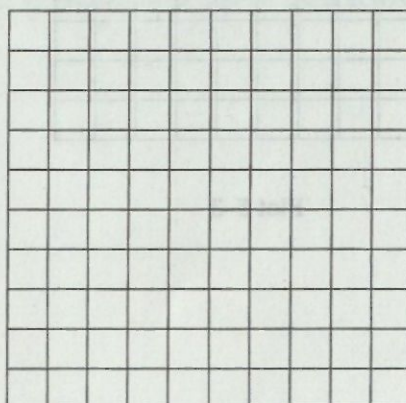

Plot 5-1

RESULTS AND CONCLUSION:

Report for
Experiment 5

ABSTRACT

FURTHER INVESTIGATION RESULTS:



Plot 5-2

APPLICATION PROBLEM RESULTS:



Plot 5-3

DATA:

Table 5-1

Component	Measured Value	Standard Value
R	2.7 kΩ	

Table 5-2

Measured values of	
Resistance	Voltage
kΩ	V
Computed Power	
P = IV	P = I ² R
mW	mW

EVALUATION AND REVIEW QUESTIONS:

1. In the first part of the experiment, you computed the power in a resistor using three different equations. Why might the results in each case be slightly different?

OBJECTIVES:

After performing this experiment, you will be able to:

2. For the circuit in Figure 5-1, assume a student accidentally set the power supply to 24 V instead of 12 V.

- (a) How much power would be dissipated in the resistor? _____
- (b) Would a $\frac{1}{4}$ W resistor be adequate for this case? _____

3. For the circuit in Figure 5-2, what was happening to the *total power* in the circuit as the resistance of R_2 was increasing? Explain your answer.

One 330 Ω , one 1.0 k Ω , one 1.5 k Ω , one 2.2 k Ω

One dc ammeter, 0–10 mA

For Further Investigation: Small light-emitting diode (T-1 or equivalent)

4. A 1.5 k Ω resistor is found to have 22.5 V across it.

- (a) What is the current in the resistor? _____
- (b) What is the power dissipated in the resistor? _____
- (c) Could a $\frac{1}{4}$ W resistor be used in this application? Explain your answer.

5. What physical characteristic determines the power rating of a resistor?

6. What is the smallest value of resistance that can be used across 10 V if the power dissipated is not to exceed 0.5 W?