

3. How many coulombs of charge do 50×10^{31} possess? 8×10^{13}
4. How many coulombs of charge does it take to make 80 microcoulombs of charge? $(8 \times 10^{-5}) / (1.6 \times 10^{-19}) = 5 \times 10^{14}$ electrons
5. Five hundred joules of energy are used to move 100C of charge through a resistor. What is the voltage across the resistor? $V = W / Q = 500J/100C = 5V$
6. How much energy does a 12V battery use to move 2.5C through a circuit? $V = W/Q$ $W = VQ$ $12 \times 2.5 = 30J$
7. A certain current source provides 100mA to a 1k Ohm load. If the resistance is decreased to 500 ohms, what is the current in the load?

.1A 1000 Ohms $V=IR$

.1x1000=100= Voltage= 100V

$I=V/R$ $100/500=.2A = 200mA$

21. (And 22) Determine the resistance values and tolerance for the following 4-band resistors:
 - a. red, violet, orange, gold: $27 \times 10^3 \pm 5\% = 27k \text{ Ohm} \pm 5\% = 25650$ (Min) to 28350 Ohms (Max)
 - b. brown, gray, red, silver: $18 \times 10^2 \pm 10\% = 1.8k \text{ Ohm} \pm 10\% = 1620$ (Min) to 1980 Ohms (Max)
 - c. brown, red, brown, gold: $12 \times 10^1 \pm 5\% = 120 \text{ Ohm} \pm 5\% = 114$ (min) to 126 Ohms (Max)
 - d. orange, blue, red, silver: $36 \times 10^2 \pm 10\% = 3.6k \text{ Ohm} \pm 10\% = 3240$ (min) to 3960 Ohms (Max)
23. Determine the color bands for each of the following 4 band, 5% values: 330 ohm, 2.2kOhm, 56kOhm, 100kOhm, and 39kOhm
 - a. Orange Orange Red Gold
 - b. Red Red Red Gold
 - c. Green Blue Orange Gold
 - d. Brown Black Yellow Gold
 - e. Orange White Orange Gold
41. Show the placement of an ammeter and a voltmeter to measure the current and the source voltage in figure 2-70