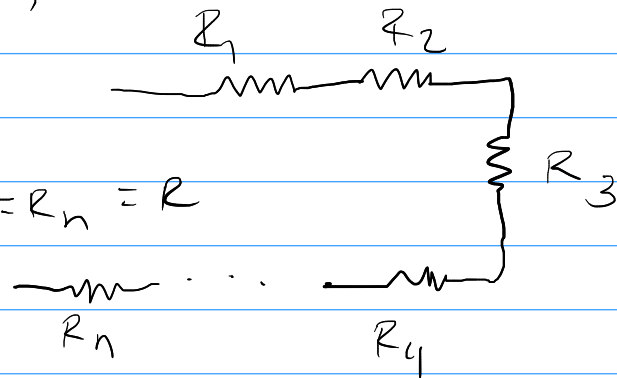


$$R_T = R_1 + R_2 + R_3 + R_4$$

$$= \sum^n R$$

$$\text{if } R_1 = R_2 = R_3 \dots = R_n = R$$




$$R_T = NR$$

$$P_{\text{delivered}} = \text{Sum of all consumed} \quad \left. \vphantom{\sum} \right\} R_T$$


$$\begin{aligned}
 R_T &= R_1 + R_2 + R_3 + R_4 \\
 &= 7\Omega + 4\Omega + 7\Omega + 7\Omega \\
 &= 25\Omega
 \end{aligned}$$

$$I = \frac{E}{R_T} = \frac{50V}{25\Omega} = 2A$$
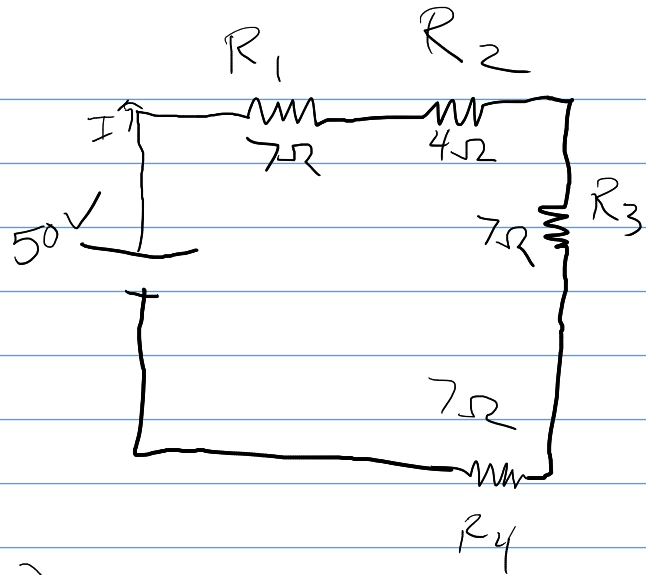
$$V_2 = I \cdot R_2 = (2A)(4\Omega) = 8V$$


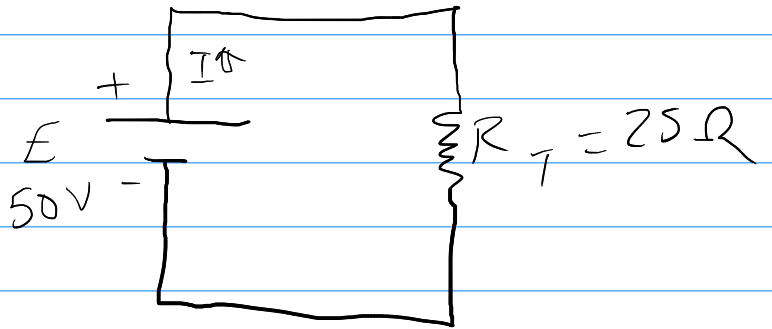
$$\begin{aligned}
 P_E &= V \cdot I \\
 &= (50V)(2A) = 100W
 \end{aligned}$$



$$P_{R_1} = V_1 I = I^2 R_1 = \frac{V_1^2}{R_1}$$

$$P_{R_1} = (2)^2 (7) = 28W$$

$$P_{R_2} = V_2 I = (8)(2) = 16W$$

$$P_{R_3} = P_{R_1} = 28W$$

$$P_{R_4} = P_{R_2} = 16W$$

$$P_{del} + P_{R_1} + P_{R_2} + P_{R_3} + P_{R_4}$$


Given R_T find I , R_1 , E

$$12k\Omega = 6k\Omega + 4k\Omega + R_1$$

$$12k\Omega = 10k\Omega + R_1$$

$$10k\Omega - 10k\Omega$$

$$R_1 = 2k\Omega$$

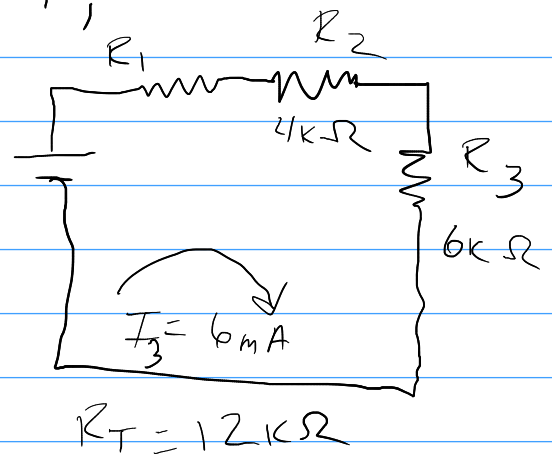

Because in series




$$I_3 = I = 6mA$$

$$E = IR$$

$$E = 6mA \cdot 12k\Omega$$



$$E = .006A \cdot 12000\Omega$$

$$E = 72V$$

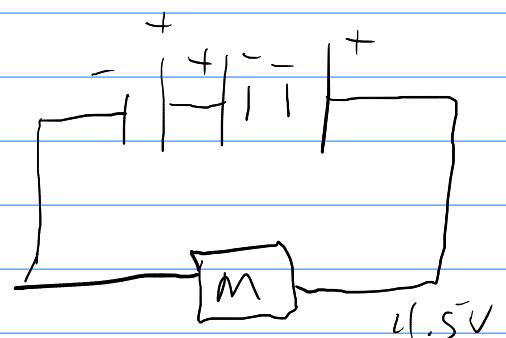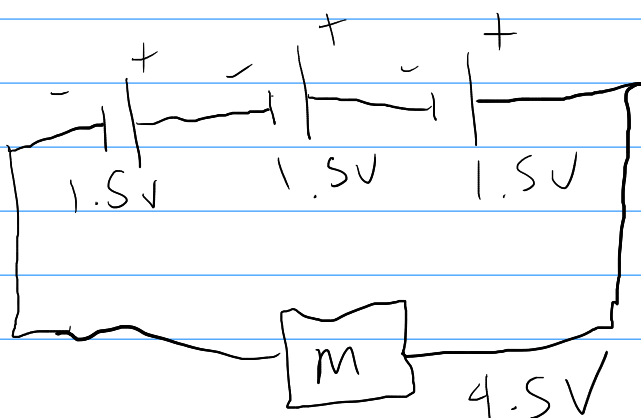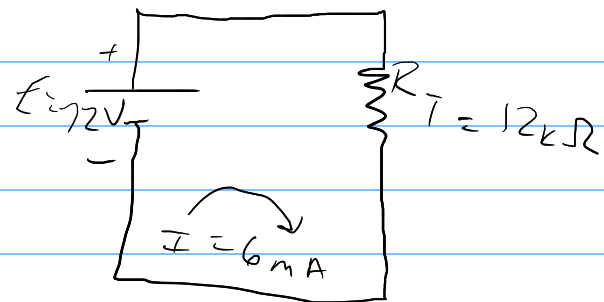

Kirchoff's Voltage law (KVL)

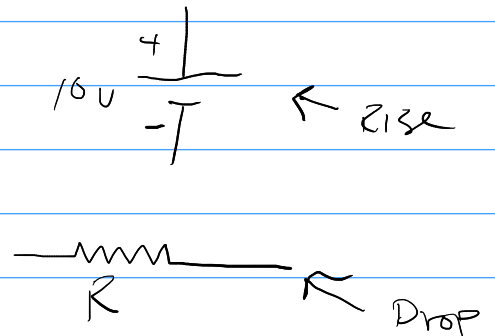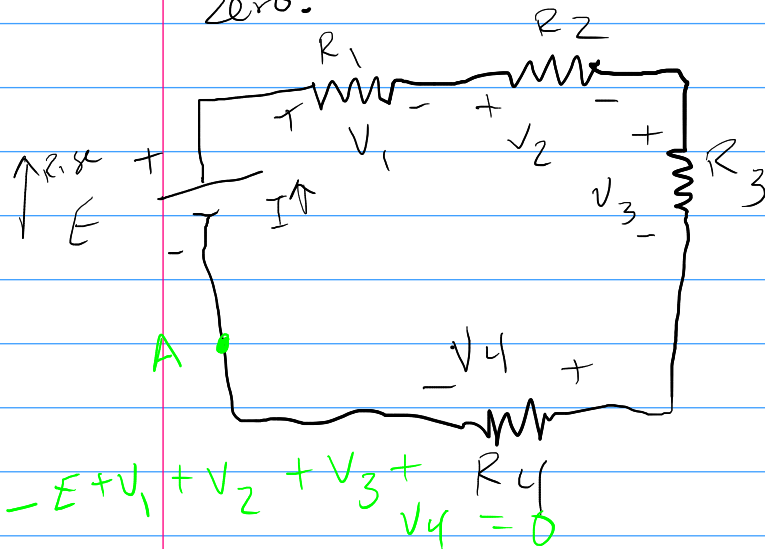
The algebraic sum of the potential rises and drops around a closed loop (Path) is zero.



Sum of all rises = Sum of all drops

Example:

Find I or V_2

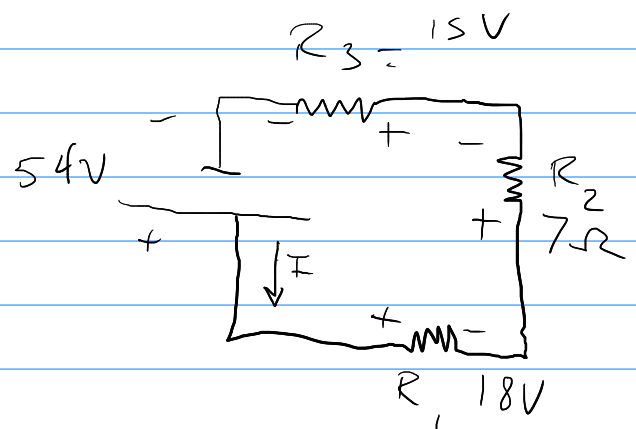

$$54V = V_1 + V_2 + V_3$$


$$= 18V + V_2 + 15V$$

$$V_2 = 21V$$

$$V_2 = I \cdot R_2 = \frac{V_2}{R_2} = \frac{21V}{7\Omega} = 3A$$

$$V_1 = I \cdot R_1 \quad R_1 = \frac{V_1}{I} = \frac{18V}{3A} = 6\Omega$$
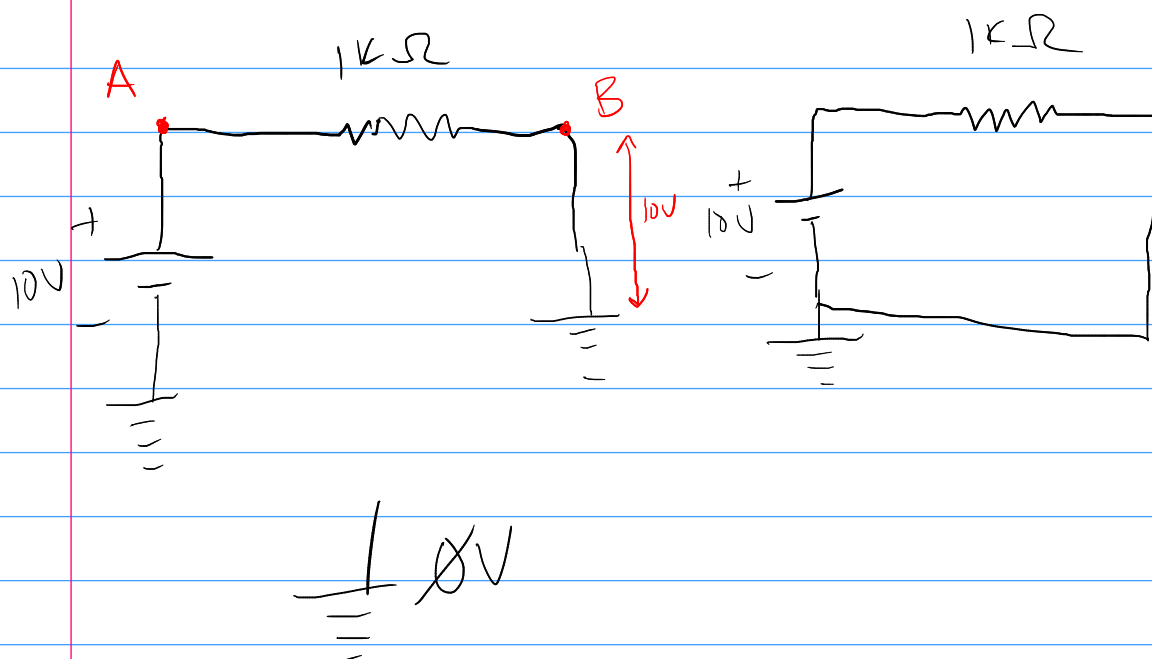
$$R_3 = \frac{V_3}{I} = \frac{15V}{3A} = 5\Omega$$



Single Subscript notation: V_a , V_b

V_a : the voltage of node A with respect to ground

Double Subscript notation: V_{ab}

V_{ab} = Voltage of point a with respect to point b

$$V_{ab} = V_a - V_b$$

