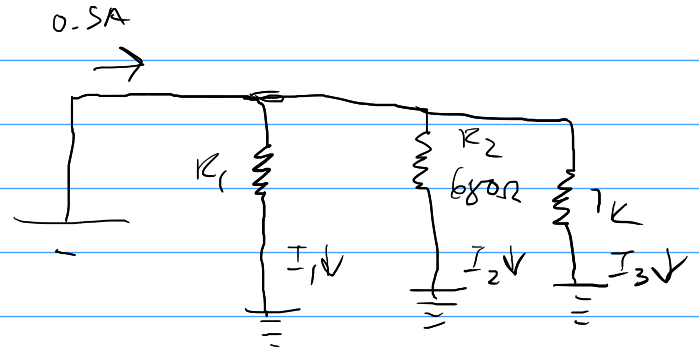


Chapter 6

28

b)




$$500 \text{ mA} = I_1 + I_2 + 100 \text{ mA}$$

$$I_2 = \frac{100}{680}$$

$$I = I_1 + I_2 + I_3$$

$$I_3 = \frac{100}{1k} = 100 \text{ mA}$$

36

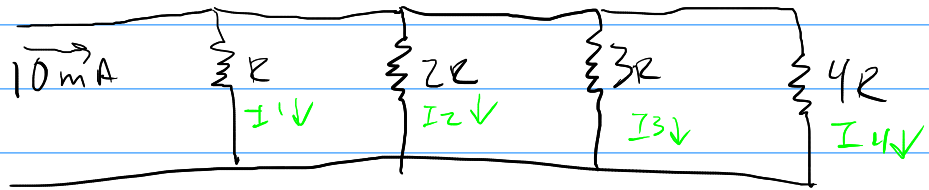

$$10 \text{ mA} = I_1 + I_2 + I_3 + I_4$$

$$I_1 = \frac{\epsilon}{R} \quad I_2 = \frac{\epsilon}{2R} \quad I_3 = \frac{\epsilon}{3R} \quad I_4 = \frac{\epsilon}{4R}$$

$$I_3 = \frac{\epsilon}{3R} = \frac{1}{3} \frac{\epsilon}{R} = \frac{1}{3} I_1 \quad I_4 = \frac{1}{4} I_1$$

$$\begin{aligned} 10 \text{ mA} &= I_1 + \frac{1}{2} I_1 + \frac{1}{3} I_1 + \frac{1}{4} I_1 \\ &= I_1 \left( 1 + \frac{1}{2} + \frac{1}{3} + \frac{1}{4} \right) \end{aligned}$$

$$R = 1 \Omega$$

$$I = \frac{R_T}{R} 10 \text{ mA}$$


## Chapter 7


### Series Parallel Circuits

Circuits that contain both series of parallel circuit configuration.

The analysis of series-parallel DC network with single source usually requires that resistance "seen" by the source ( $R_T$ ) be determined by combining series of parallel elements until a single equivalent resistance is main.

Example: Find all currents

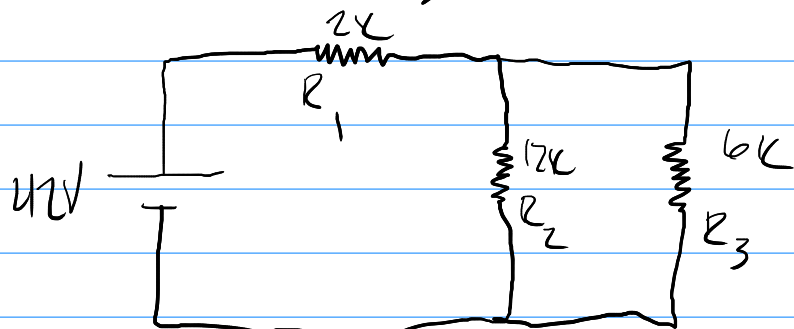

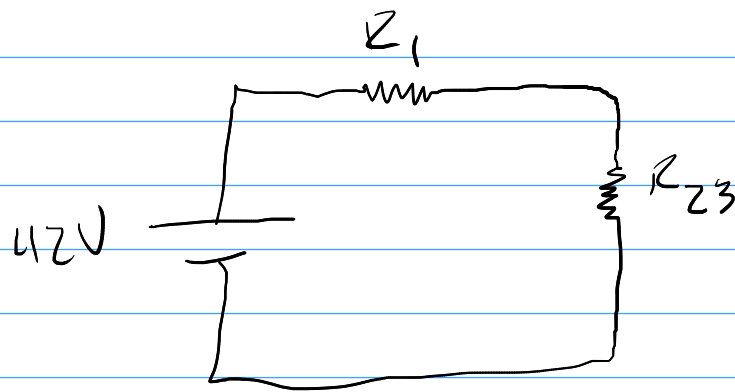


$$R_T = 2k + 4k = 6k$$

$$R_{23} = \frac{R_2 R_3}{R_2 + R_3}$$

$$\frac{(12k)(6k)}{12k + 6k} = 4k$$


$$I = \frac{42V}{6k} = 7mA$$

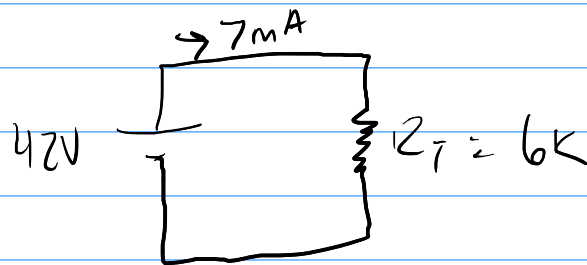

$$V_{R_1} = I \cdot R_1 = (7mA)(2k) = 14V$$

$$V_{R_{23}} = I \cdot R_{23} = (7mA)(4k) = 42V - 14V = 28V$$



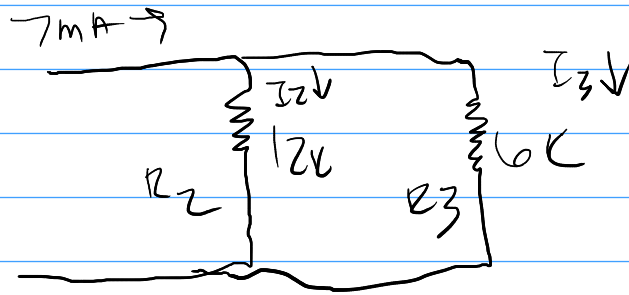
$$I_2 = \frac{28V}{12k} \quad I_3 = \frac{28V}{6k}$$




$$I_2 = \frac{6k}{6k + 12k} (7mA)$$


$$I_3 = \frac{12k}{6k + 12k} (7mA)$$

$$I_3 = I - I_2$$

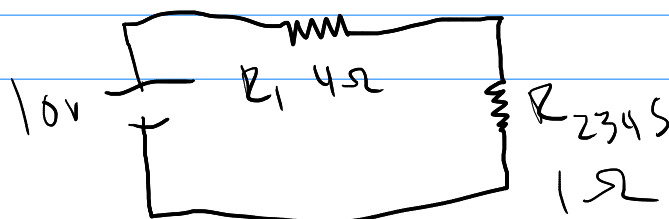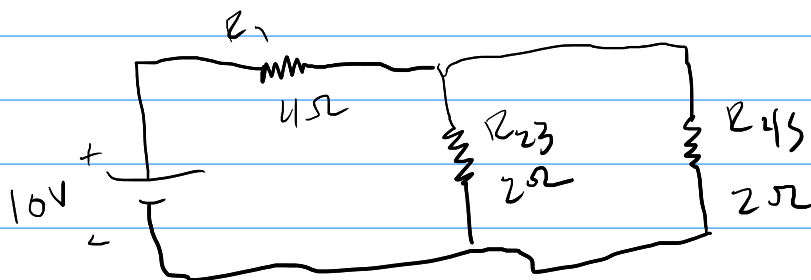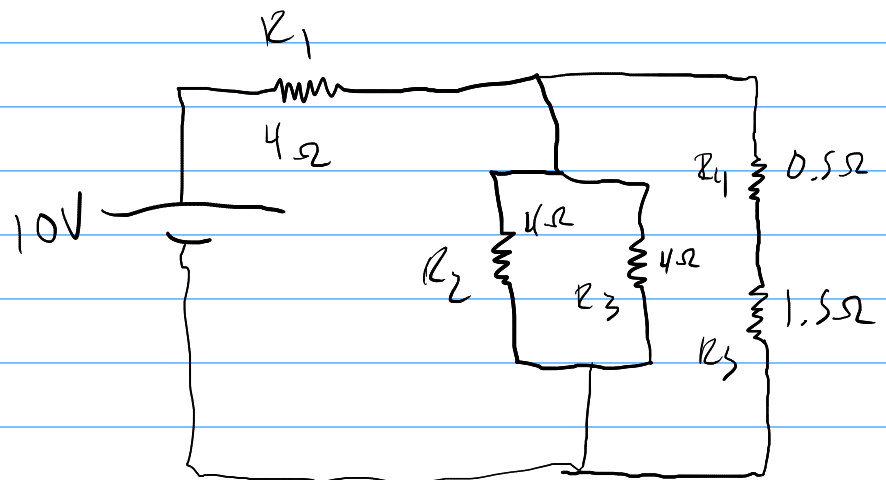

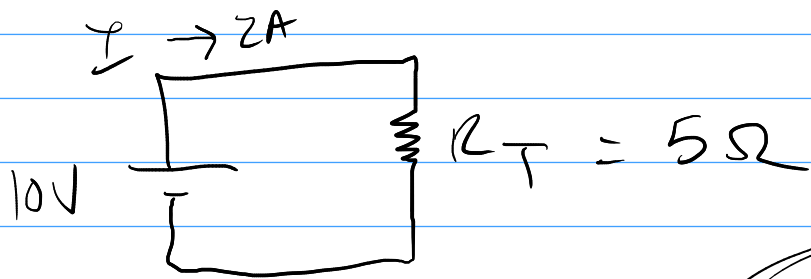

$$I_A = \frac{10V}{5\Omega} = 2A$$

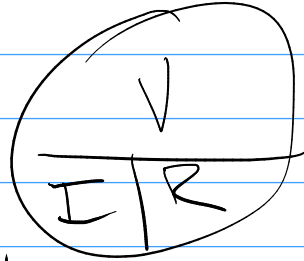

$$V_{R1} = I_A R_1 = (2A)(4\Omega) = 8V$$

$$V_{R2345} = 10 - 8 = 2V \quad \text{KVL}$$

$$= (1\Omega)(2A) = 2V \quad \text{ohm's law}$$

$$I_B = \frac{2V}{2} = 1A$$


$$I_C = \frac{2V}{2} = 1A$$

LAB 9

Parallel circuit

$$R_T = \frac{1}{\frac{1}{3.3k} + \frac{1}{4.7k} + \frac{1}{6.8k} + \frac{1}{10k}} 12V$$

$$R_{12} = \frac{R_1 R_2}{R_1 + R_2}$$

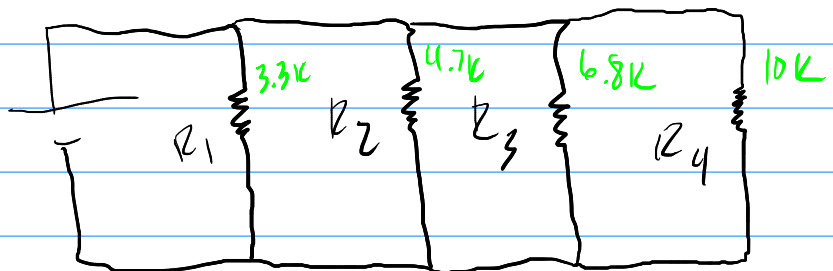

$$R_{123} = \frac{R_{12} \cdot R_3}{R_{12} + R_3}$$

$$R_{1234} = \frac{R_{123} R_4}{R_{123} + R_4}$$

$$I_T = \frac{12}{R_T}$$

$$I_1 = \frac{12}{3.3k}$$

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$I_2 = \frac{12}{4.7k}$$

$$I_3 = \frac{12}{6.8k}$$

$$I_4 = \frac{12}{10k}$$