
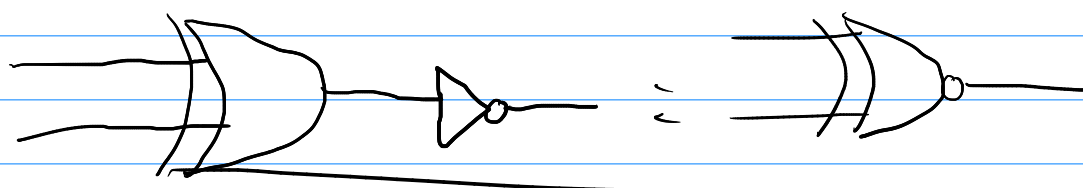


A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

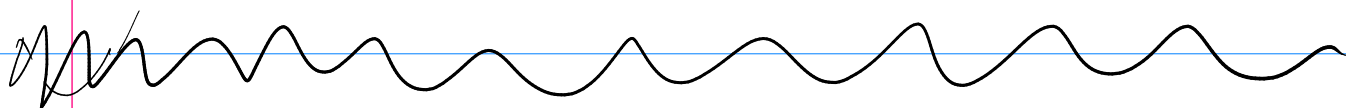

$$\begin{aligned}
 X &= A\bar{B} + \bar{A}B \\
 &= \overline{A\bar{B}} \quad \overline{\bar{A}B} \\
 &= (\bar{A} + B)(\bar{A} + \bar{B}) \\
 &= (\bar{A} + B)(A + \bar{B}) \\
 &= \cancel{\bar{A}A} + \bar{A}\bar{B} + AB + \cancel{B\bar{B}}
 \end{aligned}$$

$$\overline{X+Y} = \bar{X} \bar{Y}$$


$$\overline{XY} = \bar{X} + \bar{Y}$$

$$X = \bar{A}\bar{B} + AB$$

Implementing Combinational logic


Let's examine the following Boolean expression:

$$X = AB + CDE$$

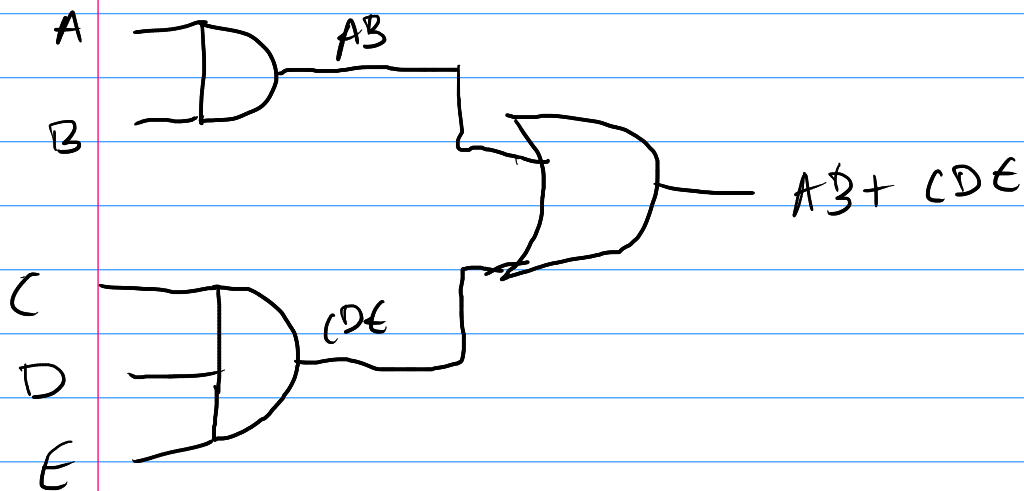

Draw logic diagram for:

$$X = AB(C\bar{D} + EF)$$

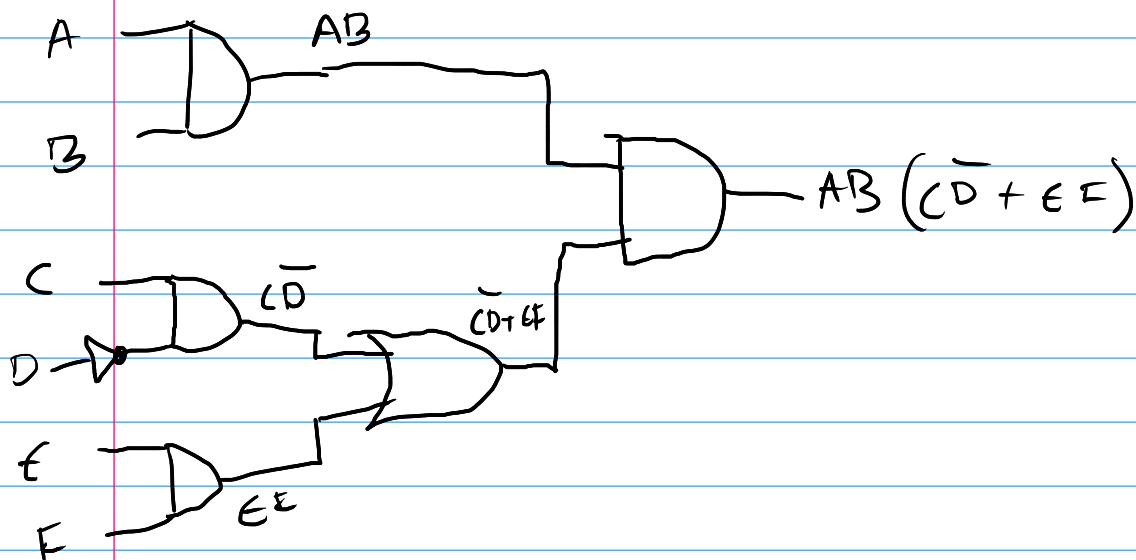

1 → Variable

0 → Variable complement

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

ABC

ABC


011

100


$\bar{A}BC$

$A\bar{B}\bar{C}$

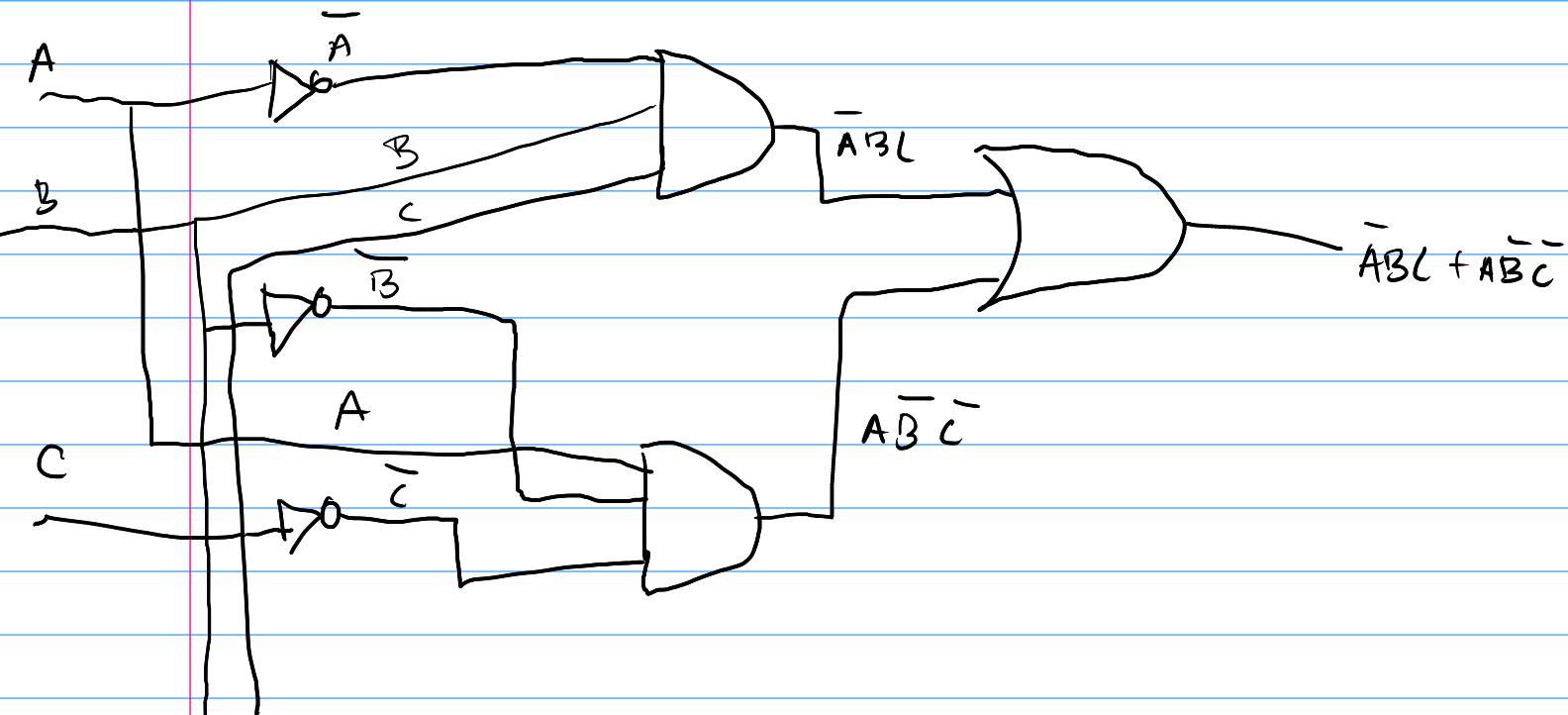SOP Expression : $\bar{A}BC + A\bar{B}\bar{C}$



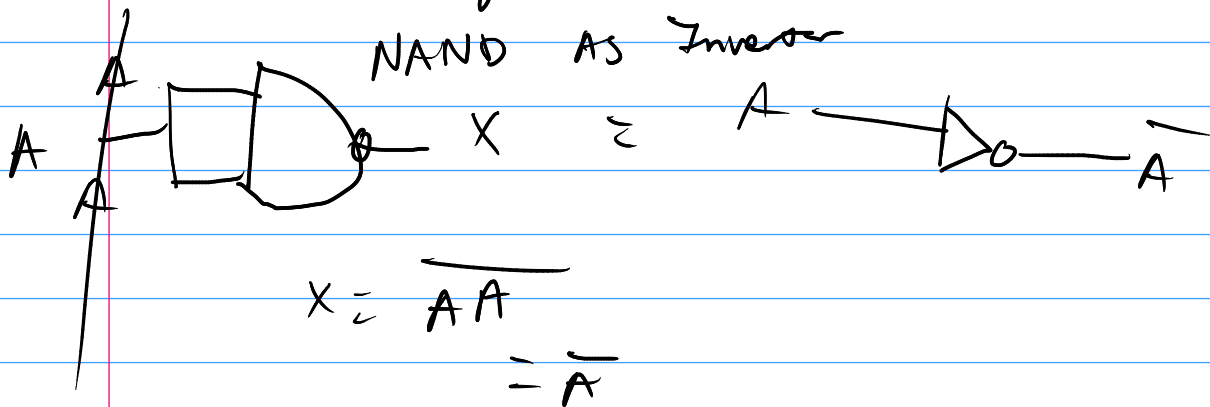
1. Nand gate as a universal logic element



$$A \cdot A = A$$

2. NAND gate as AND gate

AND = NAND + Inverter


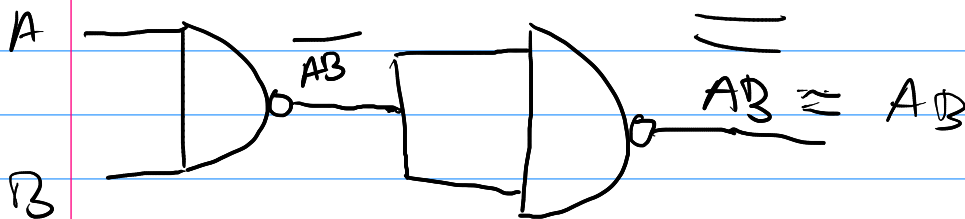


3. NAND gate as OR Gate


$$X = \overline{\overline{A+B}}$$

$$= \overline{A+B}$$
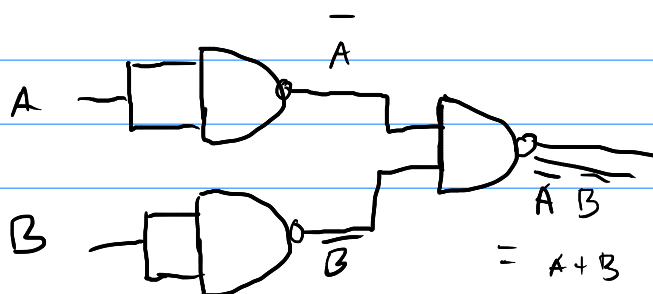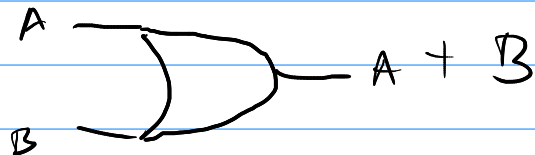
$$\overline{A+B} = \overline{A} \cdot \overline{B}$$




NAND GATE AS NOR Gate

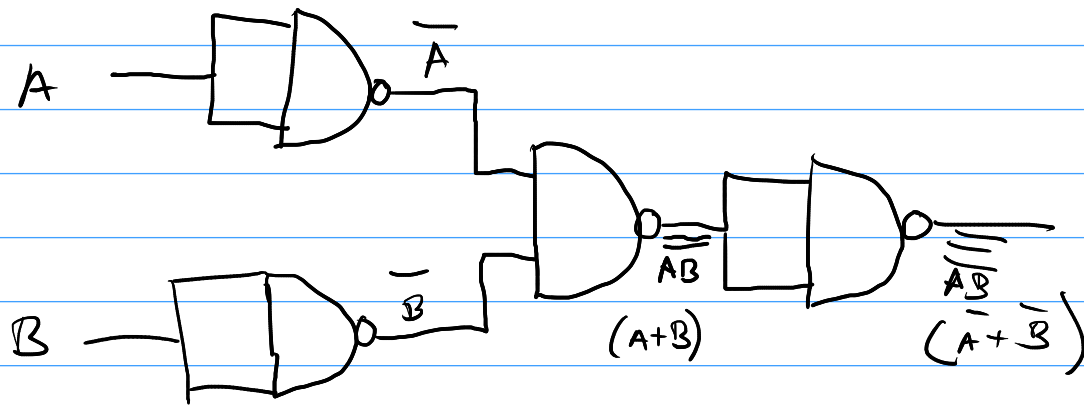


NOR Gate as an inverter

$$\overline{A+A} = \bar{A}$$

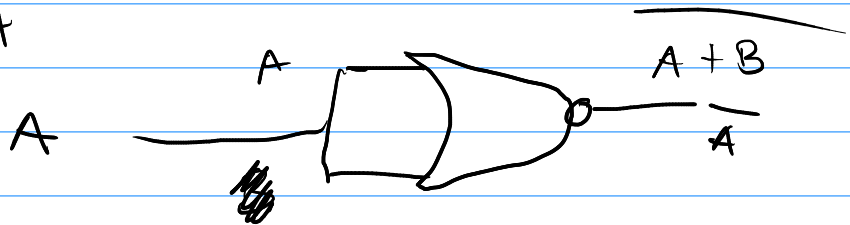

NOR GATE as an OR Gate

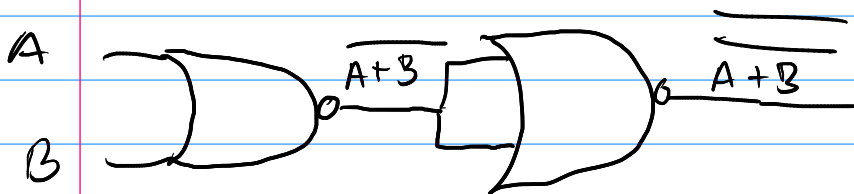

NOR GATES AS AND GATE

$$X = AB = \overline{\overline{AB}} \\ = \overline{A + B}$$

